

Lab Report 4

D-Latch, Flip Flops, 8-bit Register

ECE 238L

Kenneth Cox

April 9, 2021

Date Performed: April 9, 2021
Instructor: Professor Hamke

1 Items

D-Latch

Flip Flop

8-Bit Register

2 Feedback

The biggest problem I had was introducing my board into this lab. I have the BASYS 3, so the pins were different. Also, I wasn't able to readily identify which project part I needed, it was xc7a35tcpg236-1. Another obstacle I had to overcome was the ability to set the clock to my SW0 pin/ override the default clock.

```

) -----

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

) -- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
) --use UNISIM.VComponents.all;

) entity DLatch is
    Port ( D : in std_logic_vector (7 downto 0);
          CLK : in STD_LOGIC;
          Q : out STD_LOGIC_VECTOR (7 downto 0));
) end DLatch;

) architecture Behavioral of DLatch is

begin

)   state: process(D, CLK)

begin
)   if CLK = '1' then
        Q <= D;

)   end if;
)   end process;

) end Behavioral;

```

Figure 1: D-Latch Source

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity dLatch_bench is
-- Port ( );
end dLatch_bench;

architecture Bench of dLatch_bench is

component DLatch
    port(D, CLK: in std_logic;
         Q: out std_logic);
end component;

signal D_tb, clk_tb, Q_tb : std_logic;
constant clk_100MHZ_Period : time := 10ns;

begin
    uut: DLatch port map(D_tb, clk_tb, Q_tb);

clk_process: process
begin
    clk_tb <= '0'; wait for clk_100MHZ_Period/2;
    clk_tb <= '1'; wait for clk_100MHZ_Period/2;
end process;

stimulus: process
begin
    D_tb <= '1'; wait for 7 ns;
    D_tb <= '0'; wait for 7 ns;
end process;
end Bench;

```

Figure 2: D-Latch Test Bench

 


Figure 3: D-Latch Schematic

 


Figure 4: D-Latch Waveform

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

) -- Uncomment the following library declaration if using
  -- arithmetic functions with Signed or Unsigned values
  --use IEEE.NUMERIC_STD.ALL;

  -- Uncomment the following library declaration if instantiating
  -- any Xilinx leaf cells in this code.
  --library UNISIM;
) --use UNISIM.VComponents.all;

) entity DFFSingleBit is
    Port ( D, CLK : in STD_LOGIC;
          Q : out STD_LOGIC);
) end DFFSingleBit;

) architecture Behavioral of DFFSingleBit is

    begin

) state: process(CLK)
    begin
)     if rising_edge(CLK) then
        Q <= D;
)     end if;
) end process;
) end Behavioral;

```

Figure 5: Flip Flop Source

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity DFlipFlop_TB is
-- Port ( );
end DFlipFlop_TB;

architecture Bench of DFlipFlop_TB is
    component DFFSingleBit
        port( D, CLK : in std_logic;
              Q: out std_logic);
    end component;
    signal D_tb, CLK_tb, Q_tb : std_logic;
    constant CLK_100MHZ_Period : time := 10ns;

begin
    uut: DFFSingleBit port map( D_tb, CLK_tb, Q_tb);

    CLK_process : process
    begin
        CLK_tb <= '0'; wait for CLK_100MHZ_Period/2;
        CLK_tb <= '1'; wait for CLK_100MHZ_Period/2;
    end process;

    stimulus: process
    begin
        D_tb <= '1'; wait for 7 ns;
        D_tb <= '0'; wait for 7 ns;
    end process;

end Bench;

```

Figure 6: Flip Flop Test bench

 


Figure 7: Flip Flop Schematic

 


Figure 8: Flip Flop Waveform

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity DFlipFlop is
    Port ( D : in STD_LOGIC_VECTOR (7 downto 0);
          CLK : in STD_LOGIC;
          Q : out STD_LOGIC_VECTOR (7 downto 0));
end DFlipFlop;

architecture Behavioral of DFlipFlop is
begin

    state: process (CLK)
    begin
        if rising_edge(CLK) then
            Q(0) <= D(0);
            Q(1) <= D(1);
            Q(2) <= D(2);
            Q(3) <= D(3);
            Q(4) <= D(4);
            Q(5) <= D(5);
            Q(6) <= D(6);
            Q(7) <= D(7);
        end if;

    end process;
end Behavioral;

```

Figure 9: 8-Bit Register Source


```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.numeric_std.all;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all
entity D_FlipFlop_TB is
    -- Port( )
end D_FlipFlop_TB;

architecture bench of D_FlipFlop_TB is
    component DFlipFlop is
        Port ( D : in STD_LOGIC_VECTOR ( 7 downto 0);
              CLK : in STD_LOGIC;
              Q : out STD_LOGIC_VECTOR (7 downto 0));
    end component;

    signal D_tb, Q_tb : std_logic_vector (7 downto 0);
    signal CLK_tb : std_logic;
    constant clk_100MHZ_PERIOD : time := 10ns;

begin
    uut: DFlipFlop port map( D_tb, CLK_tb, Q_tb);

    CLK_process : process
    begin
        clk_tb <= '0'; wait for clk_100MHZ_PERIOD / 2;
        clk_tb <= '1'; wait for clk_100MHZ_PERIOD / 2;
    end process;

    stimulus: process
    begin
        D_tb <= "00000000";
        for i in 0 to 511 loop
            wait for 3 ns;
            D_tb <= std_logic_vector(unsigned(D_tb)+1);
            wait for 3 ns;
        end loop;
    end process;
end bench;

```

Figure 10: 8-Bit Register Test Bench

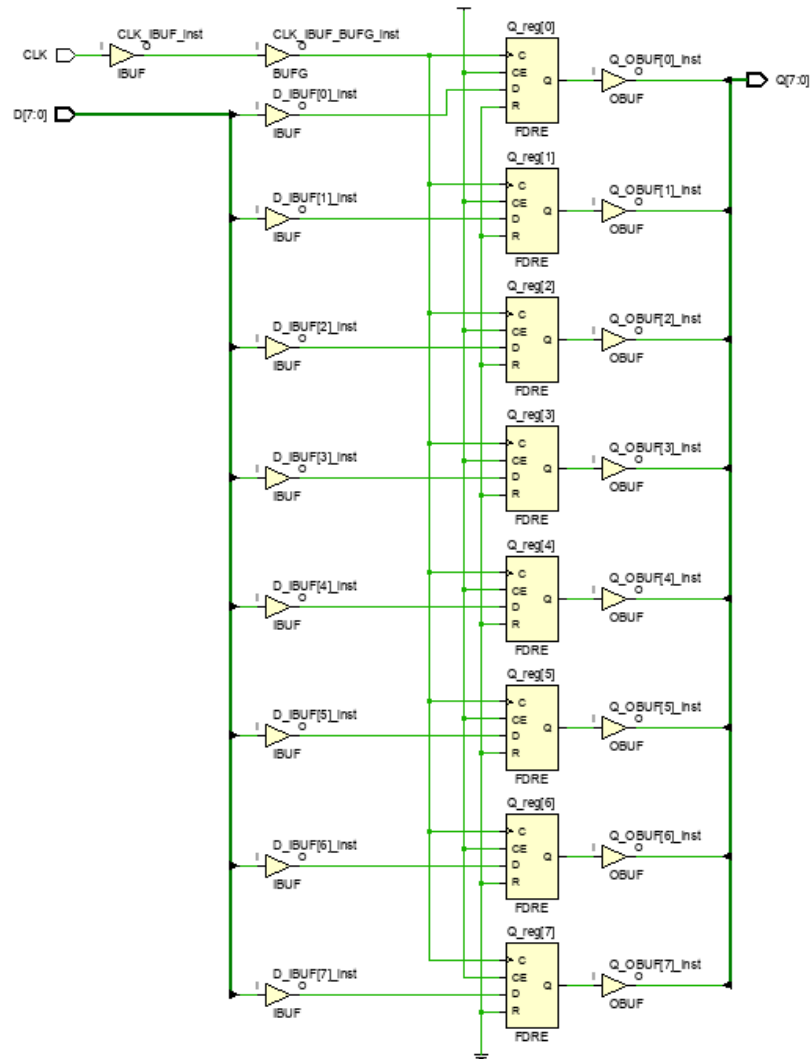


Figure 11: 8-Bit Register Schematic

```

set_property IOSTANDARD LVCMS33 [get_ports {Q[0]}]
set_property IOSTANDARD LVCMS33 [get_ports {Q[1]}]
set_property IOSTANDARD LVCMS33 [get_ports {Q[2]}]
set_property IOSTANDARD LVCMS33 [get_ports {Q[3]}]
set_property IOSTANDARD LVCMS33 [get_ports {Q[4]}]
set_property IOSTANDARD LVCMS33 [get_ports {Q[7]}]
set_property IOSTANDARD LVCMS33 [get_ports {Q[6]}]
set_property IOSTANDARD LVCMS33 [get_ports {D[0]}]
set_property IOSTANDARD LVCMS33 [get_ports {D[1]}]
set_property IOSTANDARD LVCMS33 [get_ports {D[3]}]
set_property IOSTANDARD LVCMS33 [get_ports {D[4]}]
set_property IOSTANDARD LVCMS33 [get_ports {D[5]}]
set_property IOSTANDARD LVCMS33 [get_ports {D[6]}]
set_property IOSTANDARD LVCMS33 [get_ports {D[7]}]
set_property IOSTANDARD LVCMS33 [get_ports CLK]
set_property IOSTANDARD LVCMS33 [get_ports {D[2]}]
set_property PACKAGE_PIN V17 [get_ports CLK]
set_property CLOCK_DEDICATED_ROUTE FALSE [get_nets CLK_IBUF]
create_clock -add -name sys_clk_pin -period 10.00 -waveform {0 5} [get_ports CLK]
set_property PACKAGE_PIN V2 [get_ports {D[7]}]
set_property PACKAGE_PIN W13 [get_ports {D[6]}]
set_property PACKAGE_PIN W14 [get_ports {D[5]}]
set_property PACKAGE_PIN V15 [get_ports {D[4]}]
set_property PACKAGE_PIN W15 [get_ports {D[3]}]
set_property PACKAGE_PIN W17 [get_ports {D[2]}]
set_property PACKAGE_PIN W16 [get_ports {D[1]}]
set_property PACKAGE_PIN V16 [get_ports {D[0]}]
set_property PACKAGE_PIN V13 [get_ports {Q[7]}]
set_property PACKAGE_PIN V14 [get_ports {Q[6]}]
set_property PACKAGE_PIN U14 [get_ports {Q[5]}]
set_property PACKAGE_PIN U15 [get_ports {Q[4]}]
set_property PACKAGE_PIN W18 [get_ports {Q[3]}]
set_property PACKAGE_PIN V19 [get_ports {Q[2]}]
set_property PACKAGE_PIN U19 [get_ports {Q[1]}]
set_property PACKAGE_PIN E19 [get_ports {Q[0]}]
set_property IOSTANDARD LVCMS33 [get_ports {Q[5]}]

```



Figure 12: 8-Bit Register Constraints



Figure 13: 8-Bit Register Waveform